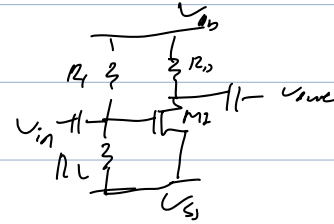


Classification of output stages.


a good circuit : $\left\{ \begin{array}{l} \text{low quiescent power dissipation} \\ \text{low distortion output.} \end{array} \right.$



$$V_{GS} = V_{GS} + v_{GS}$$


Class A amplifier
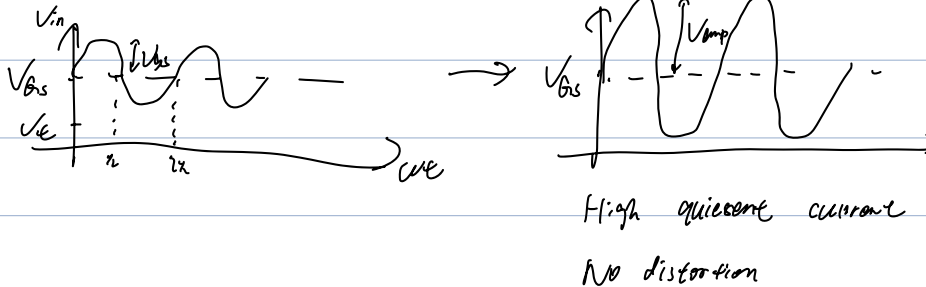
$$V_{GS} \gg V_e \quad \text{high } V_{GS}$$



Class B amplifier

$$V_{GS} = \underline{V_e} + v_{GS}$$

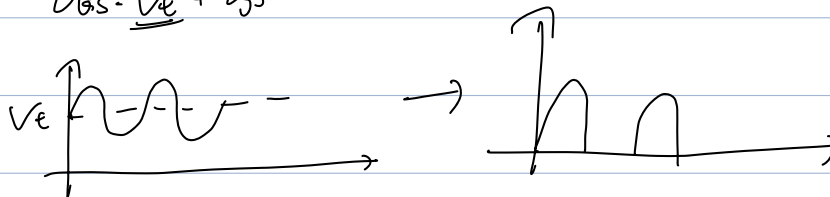


no quiescent current
distortion

Class AB


$$V_{GS} > V_e$$

$$on > 50\%$$

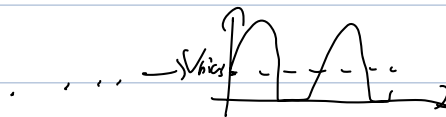

Smaller quiescent power dis
Acceptable distortion

Class C

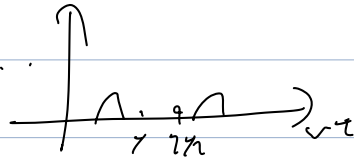

no quiescent power dissipation

High distortion.