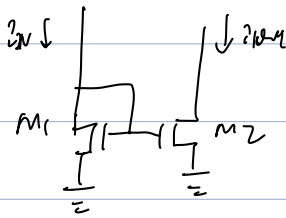


Current Mirror



$$I_{IN} = \frac{k}{2} \frac{W_1}{L_1} (V_{GS1} - V_t)^2$$

$$I_{OUT} = \frac{k}{2} \frac{W_2}{L_2} (V_{GS2} - V_t)^2$$

$$\Rightarrow \frac{I_{OUT}}{I_{IN}} = \frac{W_2/L_2}{W_1/L_1}$$

$$V_{OUT, min} = V_{IN} - V_t$$


However, it consider ccm. i.e. $I_{IN} = \frac{k}{2} \frac{W_1}{L_1} (V_{GS1} - V_t)^2 (1 + \lambda V_{DS1})$

$$I_{OUT} = \frac{k}{2} \frac{W_2}{L_2} (V_{GS2} - V_t)^2 (1 + \lambda V_{DS2})$$

$$\begin{aligned} \Rightarrow \frac{I_{OUT}}{I_{IN}} &= \frac{W_2/L_2}{W_1/L_1} \cdot \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}} = \frac{W_2/L_2}{W_1/L_1} \cdot \frac{1 + \frac{V_{OUT}}{V_A} + \frac{V_{IN}}{V_A} - \frac{V_{IN}}{V_A}}{1 + \frac{V_{IN}}{V_A}} \\ &= \frac{W_2/L_2}{W_1/L_1} \cdot \left(1 + \frac{\frac{V_{OUT}}{V_A} - \frac{V_{IN}}{V_A}}{1 + \frac{V_{IN}}{V_A}}\right) \\ &\approx \frac{W_2/L_2}{W_1/L_1} \cdot \left(1 + \frac{V_{OUT} - V_{IN}}{V_A}\right) \quad (V_A \gg V_{IN}) \end{aligned}$$

如果 $V_{IN} \neq V_{OUT}$, 仍会不匹配。

为了消除这一误差, 可以用 Cascode current mirror

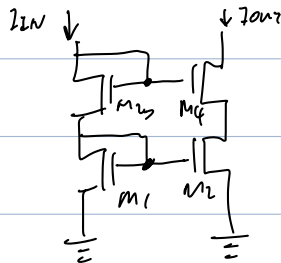


$$\begin{aligned} V_{G3} &= V_{GS3} + V_{DS1} \\ \parallel \parallel \Rightarrow \parallel \Rightarrow V_{IN} &= V_{OUT} \\ V_{G4} &= V_{GS4} + V_{DS2} \end{aligned}$$

$$V_{OUT} - (V_{OD} + V_t) \geq V_{OD}$$

$$\Rightarrow V_{OUT} \geq 2V_{OD} + V_t$$

most accurate current balance.

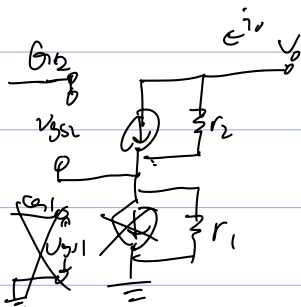


$$v_0 = (i_0 g_{m2} r_2) r_1 + i_0 r_1$$

$$v_{gs2} = 0 - i_0 r_1$$

$$\Rightarrow v_0 = (i_0 + g_{m2} i_0 r_1) r_2 + i_0 r_1$$

$$\Rightarrow \frac{v_0}{i_0} = g_{m2} r_1 r_2 + r_1 + r_2 \approx g_{m2} r_1 r_2$$

Wilson Current Mirror

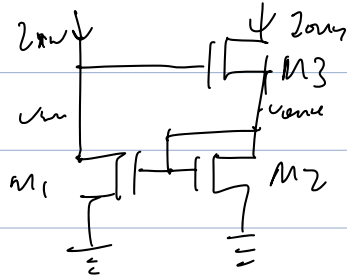

$$V_{out} - V_{in} = \text{const.}$$

Proof:

$$V_{in} = V_{GS3} + V_{DS2} = V_{GS2} + V_{DS2}$$

$$= 2V_{GS2}$$

$$V_{out} = V_{GS2}$$

$$\Rightarrow V_{out} - V_{in} = \underline{\underline{V_{GS}}}$$

Precise, but not accurate.

High R_{out} .

less transistors