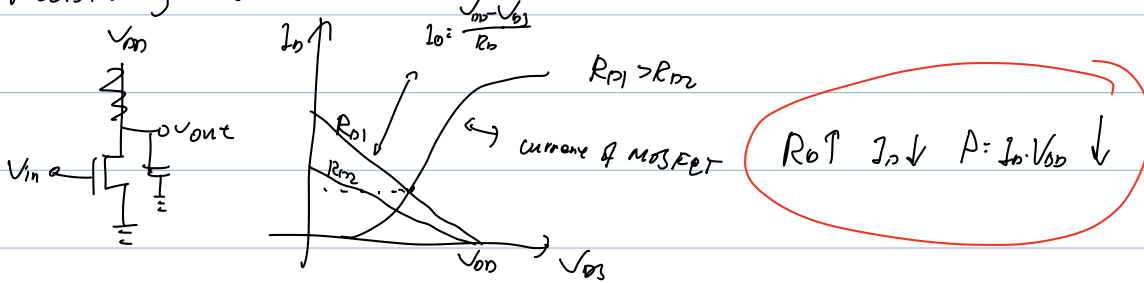


Inverter

Resistively loaded inverter



$$C \cdot \frac{dV}{dt} \Rightarrow C \frac{dV_{out}}{dt} = I_D \Rightarrow dt = C \cdot \frac{dV_{out}}{I_D}$$

$$t_{fall} = C \int_{0.1V_T}^{0.9V_T} \frac{dV_{out}}{I_D} = C \cdot \frac{0.8V_T}{\frac{1}{2}\beta(V_{DD} - V_{th})^2} = \frac{1.6C \cdot V_{DD}}{\beta(V_{DD} - V_{th})} \approx \frac{1.6C V_{DD}}{\beta}$$

与 R_D 无关


$$t_{rise} = C \cdot \int_{0.1V_T}^{0.9V_T} \frac{dV_{out}}{I_D} = C \cdot \int_{0.1V_T}^{0.9V_T} \frac{dV_{out}}{(V_{DD} - V_{out})/R_D} = -CR_D \ln(V_{DD} - V_{out}) \Big|_{0.1V_T}^{0.9V_T}$$

$$= CR_D \cdot \ln \frac{V_{DD} - 0.1V_T}{V_{DD} - 0.9V_T} = CR_D \ln 9 = \underline{\underline{2.2 CR_D}} \quad \text{与 } R_D \text{ 有关}$$



$R_D \uparrow \Rightarrow t_{rise} \uparrow$

NMOS loaded inverter

$$\frac{\beta}{2} (V_{GS} - V_{th})^2$$

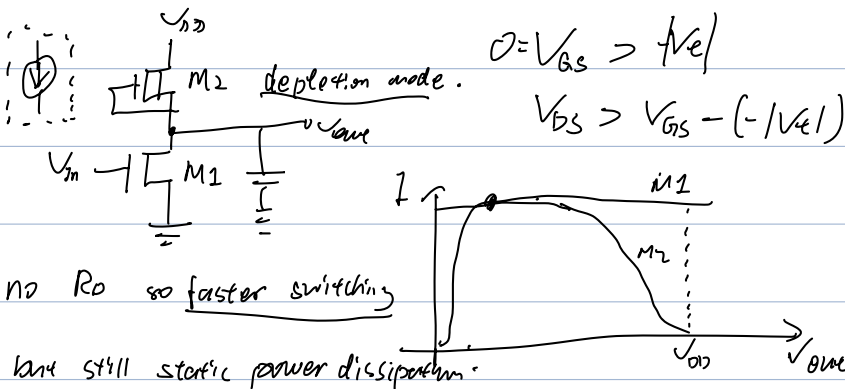

CMOS inverter.

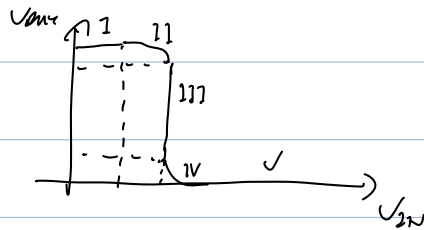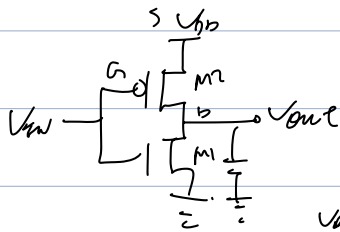

Region	NMOS	PMOS
I	cut-off $V_{in} < V_{th}$	linear $V_{DD} - V_{in} > V_{tp} , V_{DD} - V_{out} < V_{DD} - V_{in} / V_{th}$
II	saturation $V_{in} > V_{th}, V_{out} > V_{in} - V_{th}$	linear ...
III	...	...
IV	linear $V_{in} > V_{th}, V_{out} < V_{in} - V_{th}$	saturation $V_{DD} - V_{in} > V_{tp} , V_{DD} - V_{out} > V_{DD} - V_{in} / V_{tp} $
V	...	cut-off $V_{DD} - V_{in} < V_{tp} $