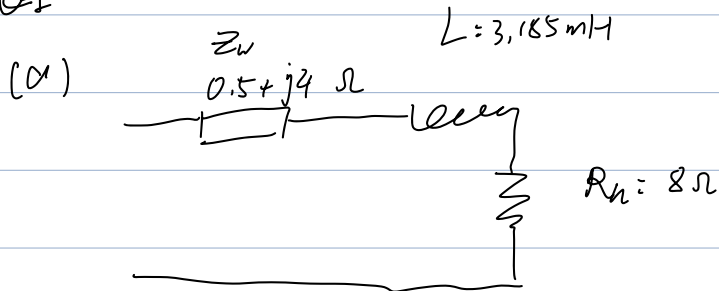


2024

Q1




(i) $\omega = 2\pi f =$

$$Z_L = j\omega L + R_L = 8 + j1 \Omega = 8.06 \angle 7.1^\circ \Omega$$

$$Z_T = Z_L + Z_S = 8.5 + j5 \Omega = 9.86 \angle 30.5^\circ \Omega$$

(ii). $I_s = \frac{V_s}{Z_T} = 12.17 \angle -30.5^\circ \text{ A}$

(iii).

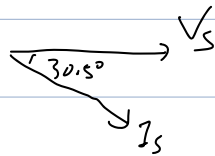

(iv). $S = |V_s| \cdot |I_s| = 1460.4 \text{ W}$


$$Q = S \sin \theta = 741.2 \text{ V}$$

$$P = S \cos \theta = 1258.3 \text{ W}$$

(v) $P_{out} = I_s^2 \cdot R_L = 1184.9 \text{ W}$

$$\text{efficiency} = \frac{P_{out}}{P} = 94.17\%$$

(b).

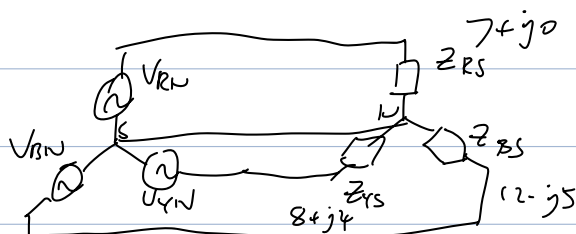

$$Z_{RS} = 7 + j0 = 7 \angle 0^\circ \Omega$$

$$Z_{YS} = 8 + j4 = 8.94 \angle 26.6^\circ \Omega$$

$$Z_{BS} = 12 - j5 = 13 \angle -22.6^\circ \Omega$$

Therefore:

$$I_R = \frac{V_{th}}{Z_{RS}} = \frac{6.6k/\sqrt{3}}{7 \angle 0^\circ} = 544.36 \angle 0^\circ A$$

$$I_Y = \frac{V_{th}}{Z_{YS}} = \frac{0.6k \angle 120^\circ / \sqrt{3}}{8.94 \angle 26.6^\circ} = 426.23 \angle -146.6^\circ A$$




$$I_B = \frac{V_{th}}{Z_{BS}} = \frac{0.6k \angle 120^\circ / \sqrt{3}}{13 \angle -22.6^\circ} = 293.12 \angle 142.6^\circ A$$

(iii). $I_{LN} = I_R + I_Y + I_B = 71.90 \angle -128.1^\circ A$

$$V_{ph} = 6.6/\sqrt{3} kV = 3.81 kV \sim$$

(iii) $\pi \left(\frac{d}{4}\right)^2 = \frac{I_{LN}}{J} \Rightarrow d = 2 \sqrt{\frac{I_{LN}}{\pi J}} = 55.2 \text{ mm}$

(iv) $P_{total} = |V_{ph}| \cdot |I_R| \cdot \cos \phi_1 + |V_{ph}| \cdot |I_Y| \cdot \cos \phi_2 + |V_{ph}| \cdot |I_B| \cdot \cos \phi_3$
 $= \frac{66k}{\sqrt{3}} \cdot (544.36 \times \cos(0^\circ) + 426.23 \times \cos(26.6^\circ) + 293.12 \times \cos(22.6^\circ))$
 $= 4.56 \text{ MW}$

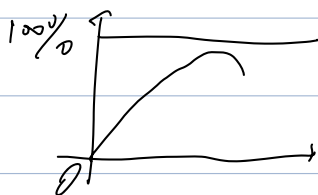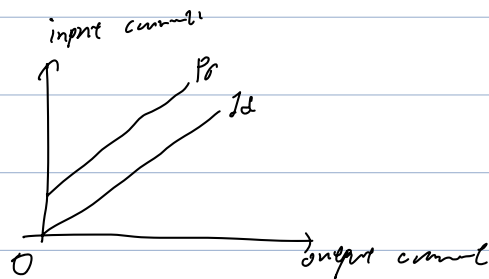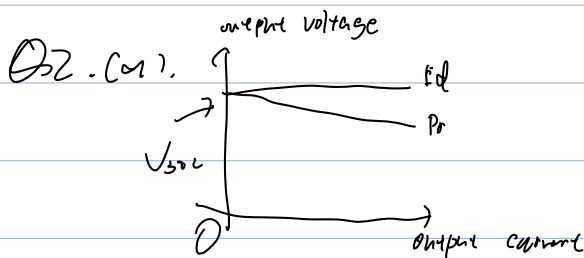


$$(b), V_{max} = \frac{2\pi}{T} N \omega B_{max} A_c \approx 4144 N \omega B_{max} A_c$$

If overvoltage,

→ magnetic saturation: if $> B_{max} \rightarrow$ distorted current waveform
 ↓
 maximum rms current increase losses

15:40:

(c) In the open circuit:

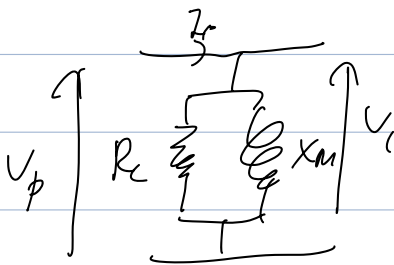

$$TR = \frac{V_p}{V_s} = \frac{240}{120} = 2$$


$$\text{From } P_p = \frac{V_p^2}{R_c} \Rightarrow R_c = \frac{V_p^2}{P_p} = 720 \Omega$$

$$S_p = I_p V_p = 144 \text{ VA}$$

$$Q_p = \sqrt{S_p^2 - P_p^2} = 119.73 \text{ VAR}$$

$$\text{From } Q_p = \frac{V_p^2}{X_m} \Rightarrow X_m = \frac{V_p^2}{Q_p} = 481.08 \Omega$$

In no short circuit:

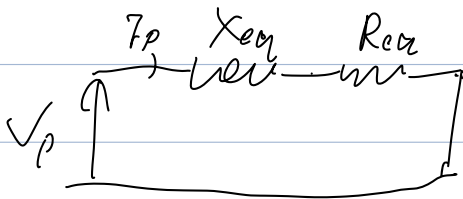


$$\text{From } P_p = I_p^2 R_{eq} \Rightarrow R_{eq} = \frac{P_p}{I_p^2} = 3.6 \Omega$$

$$Q_p = \sqrt{(V_p I_p)^2 - P_p^2} = 222.64 \text{ VAR}$$

$$\text{From } Q_p = I_p^2 X_{eq} \Rightarrow X_{eq} = \frac{Q_p}{I_p^2} = 8.90 \Omega$$
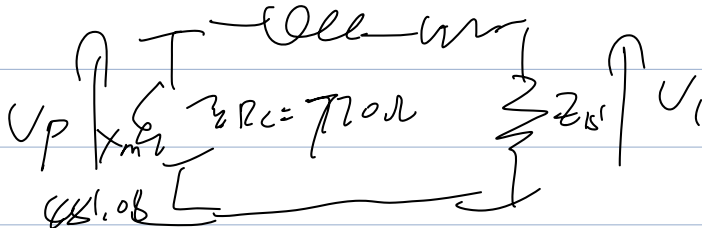
$$X_{eq} = 8.90 \Omega \quad R_{eq} = 3.6 \Omega$$



$$cd) (i). Z_{S'} = (712)^2 \cdot Z_S = 12 \Omega$$

$$Z_T = R_{eq} + Z_{S'} + jX_{eq} = 15.6 + 8.9j \Omega = 17.96 \angle 29.7^\circ \Omega$$

$$\Rightarrow I_p = \frac{V_p}{Z_T} = 13.36 \angle -29.7^\circ A$$

$$V_f = I_p \cdot Z_{S'} = 160.32 V$$

$$\Rightarrow V_2 = \frac{V_p}{T_R} = 80.16 V$$

$$Regulation = \frac{120 - 80.16}{120} \times 100\% = 33.2\%$$

$$(ii) P_{in} = |V_p| \cdot |I_p| \cdot \cos \theta = 2.785 kW$$

$$P_{out} = \frac{V_2^2}{R_L} = 2.141 kW$$

$$Efficiency = \frac{P_{out}}{P_{in}} = 76.9\%$$

ce). Let copper loss = iron loss, i.e.

$$I_p^2 \cdot R_{eq} = \frac{V_p^2}{R_c} \Rightarrow I_p = \frac{V_p}{\sqrt{R_c R_{eq}}} = 4.71 A$$

$$Z_T = \frac{V_p}{I_p} = 50.96 \Omega$$

$$Z_T \approx Z_{eq} + Z_{S'} \Rightarrow Z_{S'} = 47.36 \Omega$$

$$\Rightarrow Z_S = \frac{Z_{S'}}{712} = 11.84 \Omega$$

$$P_{out} = I_p^2 \cdot Z_{S'} = 1.05 kW$$





$$Loss = I_p^2 \cdot R_{eq} + \frac{V_p^2}{R_c} = 159.86 W$$

$$\Rightarrow Efficiency = \frac{P_{out}}{P_{out} + Loss} = 86.74\%$$

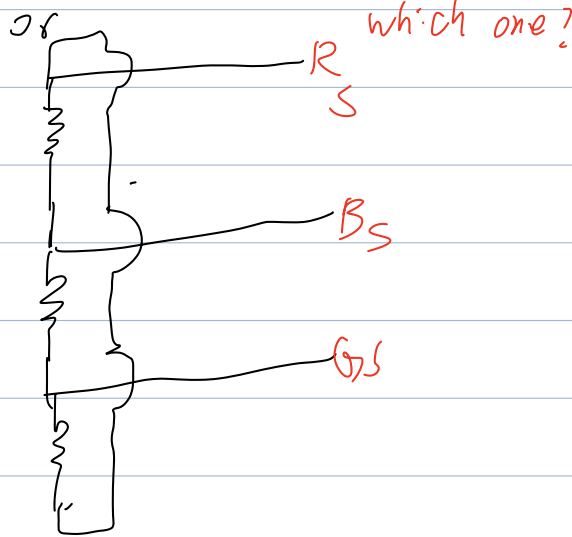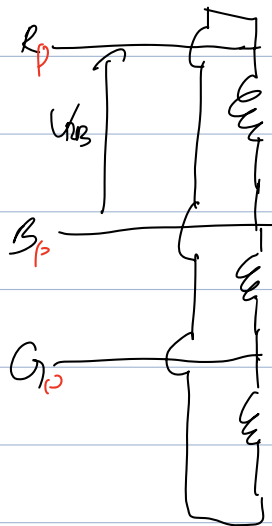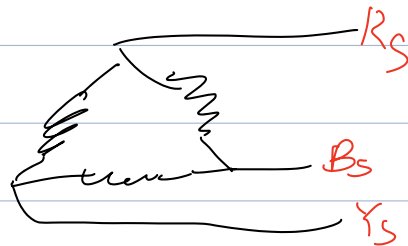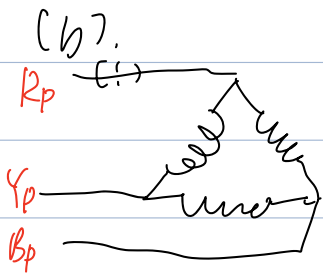(a) 1. 2. 3. single phase +
2 3phase +

pros if one broken, others could still work
cons big exp
pros compact - effi
cons

only need to replace one transformer when faulty
smaller and cheaper



(i), bank ratio $= V_{L1}/V_{L2} = 26.51$

phase ratio $= V_{ph1}/V_{ph2} = 26.51$

(ii), From $S = 3/V_{L1}/I_{ph1}$ **Keep focus!**

$\Rightarrow I_{ph1} = \frac{S}{\sqrt{3}} = 27.27 \text{ A}/3 = 9.09 \text{ A}$

$\Rightarrow I_{PL} = \sqrt{3} I_{ph1} = 47.24 \text{ A}/3 = 15.75 \text{ A}$

The current in the ^{primary} coil is $I_{ph} = 27.77 \text{ A} / 3 = 9.29 \text{ A}$

$$I_{SL} = I_{PL} \times \frac{11000}{415} = 1252.14 \text{ A} / 3 = 417.38 \text{ A}$$

$$I_{sph} = \frac{I_{SL}}{3} = 722.43 \text{ A} / 3 = 240.98 \text{ A}$$

I_{phs}



I_{phs}

(iv) $I_{SL} = I_{sph} = 722.43 \text{ A} / 3 = 240.98 \text{ A}$

$$S = \sqrt{3} |V_L| |I_{SL}| = 173.2 \text{ kVA}$$

Line or phase?

(c).

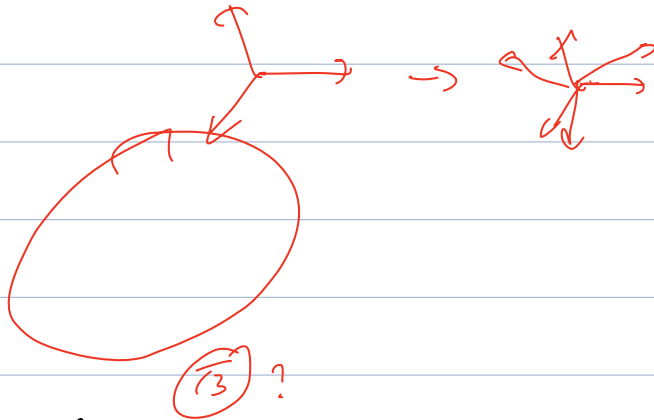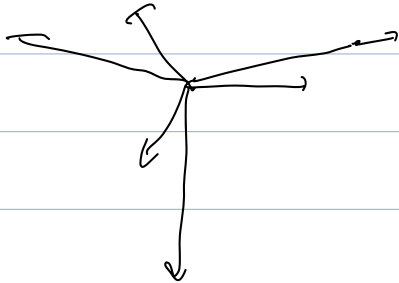

bank power = 26.51

phase power = 45.91

20